

E0 217 Project Report (Aug 2023)**Project Title:** Design, Implementation and Simulation of an 8-point FFT Circuit in 45nm CMOS**TABLE OF CONTENTS:**

S.NO	TITLE	PAGE NUMBER
1	Introduction about group members and individual Contributions	2
2	Number of clock cycles for FFT computation	2
3	Area of synthesized design	3
4	Analysis of max clock frequency	3
5	Power Consumption analysis	5
6	Energy Consumption analysis	6
7	Error Computation	6
8	Modification of FFT circuit to compute inverse FFT	8
9	Design Details and explanation of implementation	8
10	Architectural Trade-offs	11
11	References	11

E0 217 Project Report (Aug 2023)**Names and IISc Email IDs of Group Members:**


	Name	SR No.	IISc Email ID
1.	Guhan Rajasekar	22410	guhanr@iisc.ac.in
2.	Ujjwal Chaudhary	22577	ujjwalc@iisc.ac.in

Individual Contributions

	Name	Contributions
1.	Guhan Rajasekar	<ul style="list-style-type: none"> Implementation of FFT code (without control signals) Error computation between obtained and desired results Report compilation
2.	Ujjwal Chaudhary	<ul style="list-style-type: none"> Optimization of code (changing combinational blocks to sequential blocks) and making the code compatible with CLK signal and control signals like RST, WRITE, START, READY Creation of test bench and simulation of design in GTK Wave. Performed area, power and speed analysis.

Number of clock cycles per FFT computation:

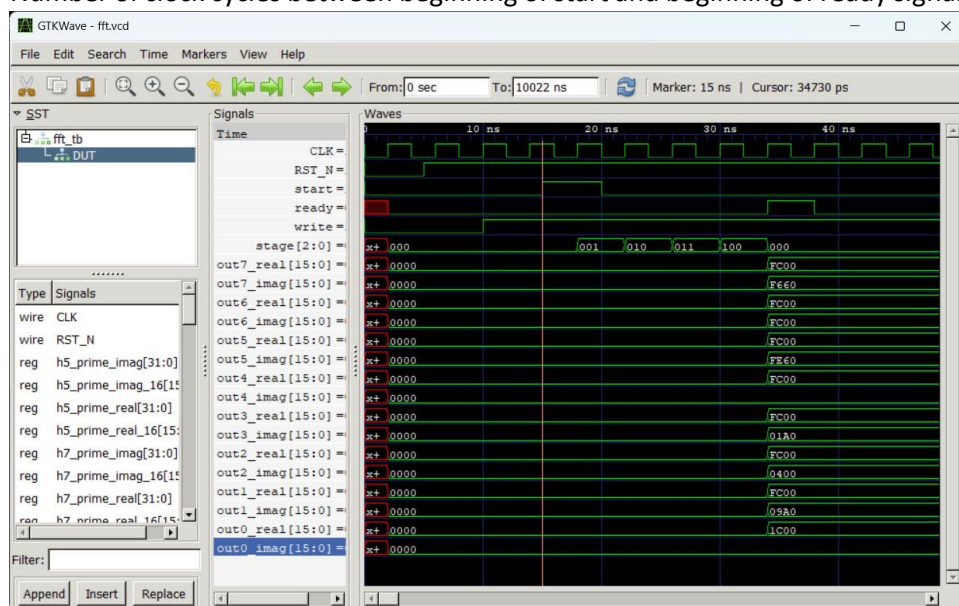- Number of clock cycles between beginning of start and beginning of ready signal = **4.75**



Area of synthesized design:

```

=== fft ===
Number of wires:          9468
Number of wire bits:      9468
Number of public wires:   1736
Number of public wire bits: 1736
Number of memories:       0
Number of memory bits:    0
Number of processes:      0
Number of cells:          7732
AND2_X1                   350
AND3_X1                    42
AOI221_X1                  88
AOI21_X1                   990
AOI221_X1                   1
AOI22_X1                    5
DFF_X1                     1156
INV_X1                     268
MUX2_X1                    736
NAND2_X1                   717
NAND3_X1                   196
NAND4_X1                    8
NOR2_X1                    515
NOR3_X1                     48
NOR4_X1                     4
OAI221_X1                   7
OAI21_X1                   544
OAI22_X1                   130
OR2_X1                     108
OR3_X1                      67
OR4_X1                      2
XNOR2_X1                   873
XOR2_X1                    877

Chip area for module '\fft': 13367.298000

```

- Area of synthesized design is **13367.298 μm^2** .

Max clock frequency supported by the synthesized design:

- Typical corner, 25°C and 1V**

```

Path Type: max
Delay    Time    Description
-----
0.00     0.00    clock CLK (rise edge)
0.00     0.00    clock network delay (ideal)
0.00     0.00    ^ _14567_/CK (DFF_X1)
0.09     0.09    v _14567_/Q (DFF_X1)
0.05     0.14    ^ _07894_/ZN (NOR2_X1)
0.03     0.17    v _07895_/ZN (NAND2_X1)
4.32     4.49    ^ _07896_/ZN (NOR2_X1)
0.04     4.53    v _08158_/ZN (OAI21_X1)
0.17     4.69    ^ _08159_/ZN (OAI22_X1)
0.00     4.69    ^ _15401_/D (DFF_X1)
4.69     4.69    data arrival time

5.00     5.00    clock CLK (rise edge)
0.00     5.00    clock network delay (ideal)
0.00     5.00    clock reconvergence pessimism
5.00     5.00    ^ _15401_/CK (DFF_X1)
-0.05    4.95    library setup time
4.95     4.95    data required time

4.95     4.95    data required time
-4.69    -4.69    data arrival time

0.26     0.26    slack (MET)

```

➤ OpenSTA> S

- This result is for typical corner, 25°C and 1V.
- Input clock signal period is 5ns.
- Here the slack period is 0.26ns.
- Supported clock period is $5\text{ns} - 0.26\text{ns} = \mathbf{4.74\text{ns}}$
- Operating frequency is **210.97 MHz**.

- **SS corner, 25°C, 1V**

```
set_power_activity -global -activity 0.5
OpenSTA> report_checks
Startpoint: _14567_ (rising edge-triggered flip-flop clocked by CLK)
Endpoint: _15401_ (rising edge-triggered flip-flop clocked by CLK)
Path Group: CLK
Path Type: max
```

Delay	Time	Description
0.00	0.00	clock CLK (rise edge)
0.00	0.00	clock network delay (ideal)
0.00	0.00	^ _14567_/CK (DFF_X1)
0.26	0.26	v _14567_/Q (DFF_X1)
0.20	0.46	^ _07894_/ZN (NOR2_X1)
0.09	0.55	v _07895_/ZN (NAND2_X1)
16.41	16.96	^ _07896_/ZN (NOR2_X1)
1.36	18.32	v _08158_/ZN (OAI21_X1)
0.85	19.17	^ _08159_/ZN (OAI22_X1)
0.00	19.17	^ _15401_/D (DFF_X1)
	19.17	data arrival time

20.00	20.00	clock CLK (rise edge)
0.00	20.00	clock network delay (ideal)
0.00	20.00	clock reconvergence pessimism
0.00	20.00	^ _15401_/CK (DFF_X1)
-0.16	19.84	library setup time
	19.84	data required time

	19.84	data required time
	-19.17	data arrival time

	0.66	slack (MET)



- This is for SS corner, 25°C and 1V.
- Input clock period is 20ns. (because this case does not support clock signal of 5ns)
- Slack period is 0.66 ns.
- Supported clock signal period is $20\text{ns} - 0.66\text{ns} = \mathbf{19.34\text{ns}}$
- Operating frequency = **51.706MHz**.

- **FF corner, 25°C, 1V**

```
set_power_activity -input -activity 0.5
set_power_activity -global -activity 0.5
OpenSTA> report_checks
Startpoint: _14567_ (rising edge-triggered flip-flop clocked by CLK)
Endpoint: _15210_ (rising edge-triggered flip-flop clocked by CLK)
Path Group: CLK
Path Type: max
```

Delay	Time	Description
0.00	0.00	clock CLK (rise edge)
0.00	0.00	clock network delay (ideal)
0.00	0.00	^ _14567_/CK (DFF_X1)
0.06	0.06	v _14567_/Q (DFF_X1)
0.03	0.08	^ _07894_/ZN (NOR2_X1)
0.01	0.10	v _07895_/ZN (NAND2_X1)
2.23	2.33	^ _07896_/ZN (NOR2_X1)
-0.01	2.32	v _09189_/ZN (NAND2_X1)
0.11	2.43	^ _09190_/ZN (OAI22_X1)
0.00	2.43	^ _15210_/D (DFF_X1)
	2.43	data arrival time

5.00	5.00	clock CLK (rise edge)
0.00	5.00	clock network delay (ideal)
0.00	5.00	clock reconvergence pessimism
0.00	5.00	^ _15210_/CK (DFF_X1)
-0.03	4.97	library setup time
	4.97	data required time

	4.97	data required time
	-2.43	data arrival time

	2.54	slack (MET)



- Input clock signal period = 5ns.
- Slack period = 2.54 ns.
- Clock period supported by the design = **2.46ns**.
- Max operating frequency at FF corner = **406.504MHz**

Power Consumption of the synthesized design:

- **Power Consumption in typical corner, 25°C and 1V:**

➤

OpenSTA> report_power					
Group	Internal Power	Switching Power	Leakage Power	Total Power	
Sequential	3.89e-03	6.85e-04	9.15e-05	4.67e-03	30.9%
Combinational	8.88e-03	1.36e-03	1.84e-04	1.04e-02	69.1%
Macro	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Pad	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Total	1.28e-02	2.05e-03	2.76e-04	1.51e-02	100.0%
	84.6%	13.6%	1.8%		

OpenSTA>

➤ The total power consumed at typical corner, 25°C and 1V is **15.1mW**.

- **Power Consumption in SS corner, 25°C and 1V.**

➤

OpenSTA> report_power					
Group	Internal Power	Switching Power	Leakage Power	Total Power	
Sequential	7.12e-04	1.26e-04	6.29e-05	9.01e-04	36.7%
Combinational	1.19e-03	2.49e-04	1.18e-04	1.55e-03	63.3%
Macro	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Pad	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Total	1.90e-03	3.75e-04	1.81e-04	2.45e-03	100.0%
	77.4%	15.3%	7.4%		

OpenSTA>

➤ Power consumed at SS corner, 25°C and 1V is **2.45mW**

- **Power Consumption in FF corner, 25°C and 1V.**

➤

OpenSTA> report_power					
Group	Internal Power	Switching Power	Leakage Power	Total Power	
Sequential	5.46e-03	8.89e-04	3.20e-04	6.67e-03	24.5%
Combinational	1.82e-02	1.78e-03	6.13e-04	2.06e-02	75.5%
Macro	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Pad	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Total	2.36e-02	2.66e-03	9.33e-04	2.72e-02	100.0%
	86.8%	9.8%	3.4%		

OpenSTA>

➤ Total power consumption at FF corner, 25°C and 1V is **27.2mW**.

Energy Consumption of synthesized design:

- Typical, 25°C, 1V, T=5ns (Image attached above)
- Typical, 25°C, 1V, T=10ns

```

ujjwal@ujjwal: ~/Desktop/ESDCS/ESDCS_project
OpenSTA> create_clock -name CLK -period 10 {CLK}
OpenSTA> report_power

```

Group	Internal Power	Switching Power	Leakage Power	Total Power	
Sequential	1.95e-03	3.43e-04	9.15e-05	2.38e-03	31.0%
Combinational	4.44e-03	6.81e-04	1.84e-04	5.31e-03	69.0%
Macro	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Pad	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Total	6.39e-03	1.02e-03	2.76e-04	7.68e-03	100.0%
	83.1%	13.3%	3.6%		

- Typical, 25°C, 1V, T=20ns

```

ujjwal@ujjwal: ~/Desktop/ESDCS/ESDCS_project
OpenSTA> create_clock -name CLK -period 20 {CLK}
OpenSTA> report_power

```

Group	Internal Power	Switching Power	Leakage Power	Total Power	
Sequential	9.73e-04	1.71e-04	9.15e-05	1.24e-03	31.0%
Combinational	2.22e-03	3.40e-04	1.84e-04	2.74e-03	69.0%
Macro	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Pad	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Total	3.19e-03	5.12e-04	2.76e-04	3.98e-03	100.0%
	80.2%	12.9%	6.9%		

Corner Case	Power Consumption (mW)	Frequency (MHz)	Energy Consumption (pJ)
Typical, 25°C, 1V	15.1	200	75.5
Typical, 25°C, 1V	7.68	100	76.8
Typical, 25°C, 1V	3.98	50	79.6

Dependence of Energy Consumption of the synthesized design on the clock frequency:

- From above mentioned table, we conclude that **energy consumption reduces as clock frequency increases.**

Maximum absolute error when computing FFT of {0, 1, 2, 3, 4, 5, 6, 7}

- Let the 8-point FFT result be denoted as $X(0)$, $X(1)$, $X(2)$, $X(3)$, $X(4)$, $X(5)$, $X(6)$ and $X(7)$
- Here a **decimal point has been added in the obtained results to indicate there are 8 bits for the fractional part, 7 bits for the decimal part and MSB is the sign bit.** This holds true for both real and imaginary parts.
- In the following calculations, $\sqrt{2}$ is considered as **1.414**.

1. X(0):

- Expected = $28 + j0$
- Obtained = $(1c.00 + j00.00)_H = 28 + j0$
- Absolute Error = 0

2. X(1)

- Expected = $-4.0 + j 9.656$
- Obtained = $(fc.00 + j09.a0)_H = -4 + j9.625$
- Absolute Error = $|(-4.0 + j 9.656) - (-4 + j9.625)| = 0.031$

3. X(2)

- Expected = $-4 + j4$
- Obtained = $(fc.00 + j04.00)_H = (-4 + j4)$
- Absolute Error = 0

4. X(3)

- Expected = $-4 + j1.656$
- Obtained = $(fc.00 + j01.a0)_H = -4 + j1.625$
- Absolute Error = $|(-4 + j1.656) - (-4 + j1.625)| = 0.031$

5. X(4)

- Expected = $-4 + j0$
- Obtained = $(fc.00 + j00.00)_H = -4 + j0$
- Absolute Error = 0

6. X(5)

- Expected = $-4 - j1.656$
- Obtained = $(fc.00 + jfe.60)_H = (-4 - j1.402)$
- Absolute Error = $|(-4 - j1.656) - (-4 - j1.402)| = 0.254$

7. X(6)


- Expected = $-4.0 - j4.0$
- Obtained = $(fc.00 + jfc.00)_H = -4 - j4$
- Absolute Error = 0

8. X(7)

- Expected = $-4 - j9.656$
- Obtained = $(fc.00 + jf6.60)_H = -4 - j9.625$
- Absolute Error = $|(-4 - j9.656) - (-4 - j9.625)| = 0.031$

Modifying the fft circuit to compute inverse fft

 
- Inverse fft can be computed using Data Swapping technique, as shown below:




-
- The real part of FFT input is fed as imaginary input to the circuit and the imaginary part of FFT is fed as real input to the circuit.
- The real portion of the output gives imaginary part of expected time domain sequence scaled by N and the imaginary part of the output gives the real part of the time domain sequence scaled by N. To get the desired outputs, we divide them by N.
- So, in addition to the existing hardware circuitry, extra circuitry will be required to scale by factor of (1/N) to get the desired time domain inverse FFT sequence.

Design Details:

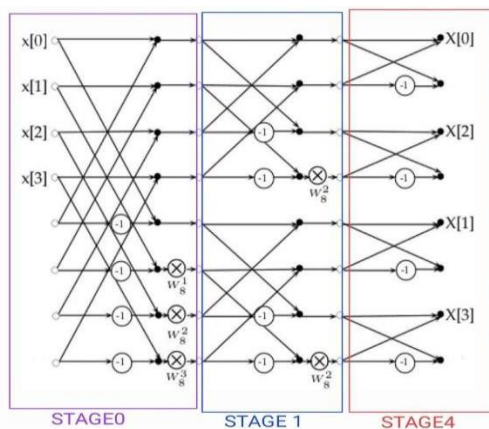
- The entire FFT computation has been divided into five stages as follows:




-
- Stage 2 and Stage 3 are used for intermediate variable computations in the code.
- But the overall FFT computation can be broadly classified into stages 0, 1 and 4.
- If the RST_N signal is low, the value 0 is written in the registers i0_real, i0_imag, i1_real, i1_imag, , i7_real, i7_imag.
- The output wires out0_real, out0_imag, out1_real, out1_imag, out7_real, out7_imag are continuously driven by the data present in the registers as shown below.

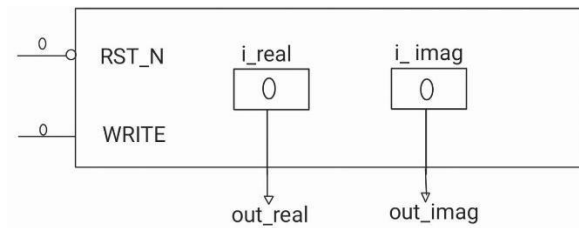

- In the above block, although only two registers are shown, there are total of 16 registers (8 for the real part and 8 for the imaginary part) and each register holds 16 bit data.
- **Storing Inputs in registers:**
 - The circuit stores inputs in registers when **write** signal is high.
 - When write signal is high, the registers i0_real ,i0_imag, i1_real,i1_imag,... ,i7_real, i7_imag will store the value held by the continuously driven wires in0_real,in0_imag,in1_real,in1_imag.....,in7_real,in7_imag respectively as shown below:

 


- Here as well only two signals in_real and in_imag are shown for brevity of block diagram.
- But there are 16 wires (8 for real and 8 for imaginary parts) that are continuously driven.
- Computation commences when **start** signal is high.
- The value stored by 2-bit register variable named **stage** indicates the stage of FFT computation.
- **Stage 0 computations:**
 - The contents in i0_real, i0_imag,.....,i7_real,i7_imag act as inputs for stage 0 computations.
 - The registers g_real[0], g_imag[0], g_real[1],g_imag[1].....,g_real[7],g_imag[7] store the results of stage 0.

 

- Once again for brevity, not all the registers of stage 0 are shown.
- There are 16 registers. 8 registers hold the real part of stage 0 results and 8 registers hold the imaginary part of stage 0 results .
- Stage 0 computations is based on the formula obtained from the butterfly diagram.
- Once stage 0 computations are done, the content of **stage register** is incremented by 1 to go to the next stage.

- **Stage 1 computations**

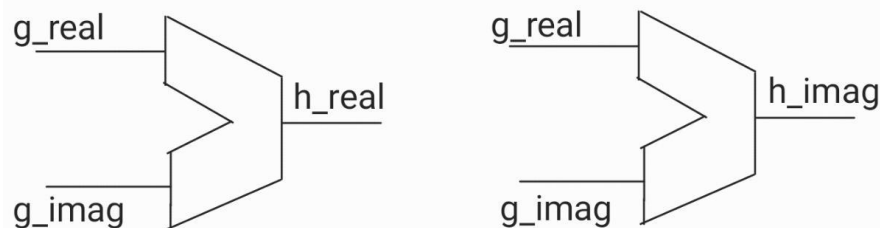- For stage 1 computations, the contents of the registers $g_real[0]$, $g_imag[0]$, $g_real[1]$, $g_imag[1]$, ..., $g_real[7]$, $g_imag[7]$ will be the inputs and the results are stored in the registers $h_real[0]$, $h_real[1]$, ..., $h_real[7]$, $h_imag[0]$, ..., $h_imag[7]$



-
- The computations are based on the equations obtained from the butterfly diagram.

- **Stage 2 computations**


- In this stage , the registers temp0, temp1 ,temp2 and temp3 are populated as follows:
 - $temp0 = h_real[5] + h_imag[5]$
 - $temp1 = h_imag[5] - h_real[5]$
 - $temp2 = h_imag[7] - h_real[7]$
 - $temp3 = -(h_imag[7] + h_real[7])$
- These calculations aid in the computation of the final result.
- Once the above calculations are done, contents of the stage register is incremented by 1 and we go to the next stage.

- **Stage 3 computations**

- In this stage, the contents of temp0, temp1, temp2, temp3 are multiplied with 0.707 (hard coded in binary in the code) .
- Then content of the stage register is incremented and we go to the final stage.

- **Stage 4 computations:**

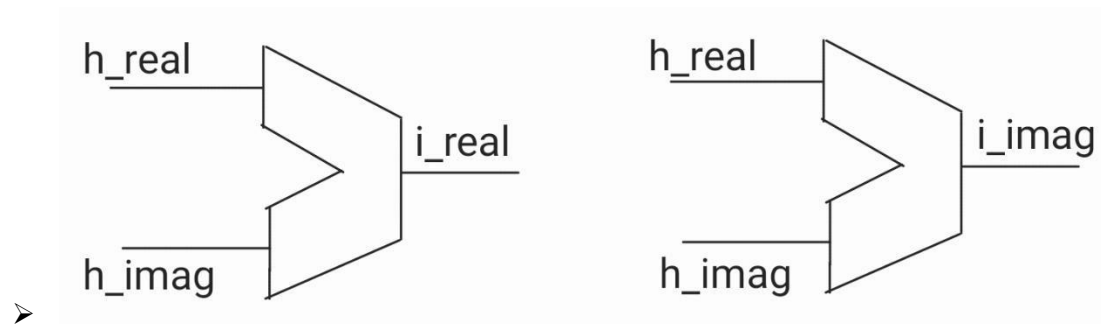- Here the contents of $h_real[0]$, $h_imag[0]$, $h_real[1]$, $h_imag[1]$, ..., $h_real[7]$, $h_imag[7]$ act as inputs and the final output is stored in the registers $i_real[0]$, $i_imag[0]$, $i_real[1]$, $i_imag[1]$, ..., $i_real[7]$, $i_imag[7]$.



- The wires out0_real , out0_imag, out1_real, out1_imag,.....out7_real,out7_imag are continuously driven by the contents in these registers. Hence at any point of time, the output at that instant is present in these output wires.

Architectural Trade-offs

- In this FFT implementation, focus is low latency.
- Hence the inbuilt multiplication function has been used with the ' * ' symbol to get faster multiplication results that are required at the intermediate stages.
- This comes at the cost of more area and power consumption.
- As an addition, pipelining can be implemented if we want to improve throughput.

Verilog Code to implement fft:

```

module fft(CLK, RST_N, write, start, in0_real , in0_imag, in1_real, in1_imag,
in2_real ,in2_imag, in3_real ,in3_imag, in4_real ,in4_imag, in5_real ,in5_imag,
in6_real ,in6_imag, in7_real ,in7_imag, ready, out0_real ,out0_imag, out1_real,
out1_imag, out2_real ,out2_imag, out3_real ,out3_imag, out4_real ,out4_imag,
out5_real ,out5_imag, out6_real ,out6_imag, out7_real ,out7_imag);

    input CLK, RST_N;
    input write, start;
    input wire signed [15:0] in0_real ,in0_imag;
    input wire signed [15:0] in1_real ,in1_imag;
    input wire signed [15:0] in2_real ,in2_imag;
    input wire signed [15:0] in3_real ,in3_imag;
    input wire signed [15:0] in4_real ,in4_imag;
    input wire signed [15:0] in5_real ,in5_imag;
    input wire signed [15:0] in6_real ,in6_imag;
    input wire signed [15:0] in7_real ,in7_imag;
    output reg ready;
    output wire signed [15:0] out0_real ,out0_imag;
    output wire signed [15:0] out1_real ,out1_imag;
    output wire signed [15:0] out2_real ,out2_imag;
    output wire signed [15:0] out3_real ,out3_imag;
    output wire signed [15:0] out4_real ,out4_imag;
    output wire signed [15:0] out5_real ,out5_imag;
    output wire signed [15:0] out6_real ,out6_imag;
    output wire signed [15:0] out7_real ,out7_imag;

    reg signed [15:0] i0_real, i0_imag;
    reg signed [15:0] i1_real, i1_imag;
    reg signed [15:0] i2_real, i2_imag;
    reg signed [15:0] i3_real, i3_imag;
    reg signed [15:0] i4_real, i4_imag;
    reg signed [15:0] i5_real, i5_imag;
    reg signed [15:0] i6_real, i6_imag;
    reg signed [15:0] i7_real, i7_imag;
    reg [2:0] stage;

    reg signed [15:0] g_real [0:7]; // Declare g_real as an array of registers to store real
part of stage 1 results
    reg signed [15:0] g_imag [0:7]; // Declare g_imag as an array of registers to store imag
part of stage 1 results
    reg signed [15:0] h_real [0:7]; // Declare h_real as an array of registers to store real
part of stage 2 results
    reg signed [15:0] h_imag [0:7]; // Declare h_imag as an array of registers to store imag
part of stage 2 results
    reg signed [15:0] i_real [0:7]; // Declare i_real as an array of registers to store real
part of stage 3 results
    reg signed [15:0] i_imag [0:7]; // Declare i_imag as an array of registers to store imag
part of stage 3 results

```

```

reg signed [15:0] temp1,temp2,temp3,temp0;
reg signed [31:0] h5_prime_real; // 32 bit register to store real part of h[5] * (W8 ^ 1)
reg signed [31:0] h5_prime_imag; // 32 bit register to store imag part of h[5] * (W8 ^ 1)
reg signed [31:0] h7_prime_real; // 32 bit register to store real part of h[7] * (W8 ^ 3)
reg signed [31:0] h7_prime_imag; // 32 bit register to store imag part of h[7] * (W8 ^ 3)

reg signed [15:0] h5_prime_real_16; // 16 bit register to store real part of h[5] * (W8 ^ 1)
reg signed [15:0] h5_prime_imag_16; // 16 bit register to store imag part of h[5] * (W8 ^ 1)
reg signed [15:0] h7_prime_real_16; // 16 bit register to store real part of h[7] * (W8 ^ 3)
reg signed [15:0] h7_prime_imag_16; // 16 bit register to store imag part of h[7] * (W8 ^ 3)

always @(posedge CLK) begin
    if (~RST_N) begin
        ready <= 1'b0;
        stage <= 2'b00;
        i_real[0] <= 0; i_imag[0]<=0;
        i_real[1] <= 0; i_imag[1]<=0;
        i_real[2] <= 0; i_imag[2]<=0;
        i_real[3] <= 0; i_imag[3]<=0;
        i_real[4] <= 0; i_imag[4]<=0;
        i_real[5] <= 0; i_imag[5]<=0;
        i_real[6] <= 0; i_imag[6]<=0;
        i_real[7] <= 0; i_imag[7]<=0;
    end
    else begin
        if (start) begin
            g_real[0] <= i0_real + i4_real;
            g_imag[0] <= i0_imag + i4_imag;
            g_real[1] <= i0_real - i4_real;
            g_imag[1] <= i0_imag - i4_imag;
            g_real[2] <= i2_real + i6_real;
            g_imag[2] <= i2_imag + i6_imag;
            g_real[3] <= i2_real - i6_real;
            g_imag[3] <= i2_imag - i6_imag;
            g_real[4] <= i1_real + i5_real;
            g_imag[4] <= i1_imag + i5_imag;
            g_real[5] <= i1_real - i5_real;
            g_imag[5] <= i1_imag - i5_imag;
            g_real[6] <= i3_real + i7_real;
            g_imag[6] <= i3_imag + i7_imag;
            g_real[7] <= i3_real - i7_real;
            g_imag[7] <= i3_imag - i7_imag;
            stage <= 3'b01;
        end
        else if (stage > 0 ) begin

```

```

case(stage)
  3'b001:begin
    h_real[0] <= g_real[0] + g_real[2];           // h0_real = g0_real + g2_real
    h_imag[0] <= g_imag[0] + g_imag[2];           // h0_imag = g0_imag + g2_imag
    h_real[1] <= g_real[1] + g_imag[3];           // h1_real = g1_real - (j*g3_real)
    h_imag[1] <= g_imag[1] - g_real[3];           // h1_imag = g1_imag - (j*g3_imag)
    h_real[2] <= g_real[0] - g_real[2];           // h2_real = g0_real - g2_real
    h_imag[2] <= g_imag[0] - g_imag[2];           // h2_imag = g0_imag - g2_imag
    h_real[3] <= g_real[1] - g_imag[3];           // h3_real = g1_real + (j*g3_real)
    h_imag[3] <= g_imag[1] + g_real[3];           // h3_imag = g1_imag + (j*g3_imag)
    h_real[4] <= g_real[4] + g_real[6];           // h4_real = g4_real + g6_real
    h_imag[4] <= g_imag[4] + g_imag[6];           // h4_imag = g4_imag + g6_imag
    h_real[5] <= g_real[5] + g_imag[7];           // h5_real = g5_real - (j*g7_real)
    h_imag[5] <= g_imag[5] - g_real[7];           // h5_imag = g5_imag - (j*g7_imag)
    h_real[6] <= g_real[4] - g_real[6];           // h6_real = g4_real - g6_real
    h_imag[6] <= g_imag[4] - g_imag[6];           // h6_imag = g4_imag - g6_imag
    h_real[7] <= g_real[5] - g_imag[7];           // h7_real = g5_real + (j*g7_real)
    h_imag[7] <= g_imag[5] + g_real[7];           // h7_imag = g5_imag + (j*g7_imag)
  end
  3'b010:begin
    temp0 <= h_real[5] + h_imag[5];
    temp1 <= h_imag[5] - h_real[5];
    temp2 <= h_imag[7] - h_real[7];
    temp3 <= -(h_imag[7] + h_real[7]);
  end
  3'b011:begin
    h5_prime_real <= temp0 * 16'b0000000010110100;
    h5_prime_imag <= temp1 * 16'b0000000010110100;
    h7_prime_real <= temp2 * 16'b0000000010110100;
    h7_prime_imag <= temp3 * 16'b0000000010110100;
  end
  3'b100:begin
    i_real[0] <= h_real[0] + h_real[4]; // i0_real = h0_real + h4_real
    i_imag[0] <= h_imag[0] + h_imag[4]; // i0_imag = h0_imag + h4_imag
    i_real[1] <= h_real[1] + h5_prime_real_16; // i1_real = h[1]_real + Re((W8 ^
1)*h[5])
    i_imag[1] <= h_imag[1] + h5_prime_imag_16; // i1_imag = h[1]_imag + Im((W8 ^
1)*h[5])
    i_real[2] <= h_real[2] + h_imag[6]; // i2_real = h2_real - (j*h6_real)
    i_imag[2] <= h_imag[2] - h_real[6]; // i2_imag = h2_imag - (j*h6_imag)
    i_real[3] <= h_real[3] + h7_prime_real_16; // i3_real = h[3]_real +
Re((W8^3)*h[7])
    i_imag[3] <= h_imag[3] + h7_prime_imag_16; // i3_imag = h[3]_imag +
Im((W8^3)*h[7])
    i_real[4] <= h_real[0] - h_real[4]; // i4_real = h0_real - h4_real
    i_imag[4] <= h_imag[0] - h_imag[4]; // i4_imag = h0_imag - h4_imag
    i_real[5] <= h_real[1] - h5_prime_real_16; // i5_real = h[1]_real -
Re((W8^1)*h[5])
    i_imag[5] <= h_imag[1] - h5_prime_imag_16; // i5_imag = h[1]_imag -
Im((W8^1)*h[5])

```

```

        i_real[6] <= h_real[2] - h_imag[6]; // i6_real = h2_real + (j*h6_real)
        i_imag[6] <= h_imag[2] + h_real[6]; // i6_imag = h2_imag + (j*h6_imag)
        i_real[7] <= h_real[3] - h7_prime_real_16; // i7_real = h[3]_real -
Re((W8^3)*h[7])
        i_imag[7] <= h_imag[3] - h7_prime_imag_16; // i7_imag = h[3]_imag -
Im((W8^3)*h[7])
        ready <= 1'b1;
    end
endcase

    if(stage == 3'b100) begin
        stage <= 2'b00;
    end
    else begin
        stage <= stage + 2'b01;
    end

end
else begin
    if (write) begin
        i0_real<= in0_real; i0_imag <= in0_imag;
        i1_real<= in1_real; i1_imag <= in1_imag;
        i2_real<= in2_real; i2_imag <= in2_imag;
        i3_real<= in3_real; i3_imag <= in3_imag;
        i4_real<= in4_real; i4_imag <= in4_imag;
        i5_real<= in5_real; i5_imag <= in5_imag;
        i6_real<= in6_real; i6_imag <= in6_imag;
        i7_real<= in7_real; i7_imag <= in7_imag;
    end
    ready <= 1'b0;
end
end
end

always@(*) begin
    h5_prime_real_16 <= h5_prime_real[23:8];
    h5_prime_imag_16 <= h5_prime_imag[23:8];
    h7_prime_real_16 <= h7_prime_real[23:8];
    h7_prime_imag_16 <= h7_prime_imag[23:8];
end

assign out0_real = i_real[0]; assign out0_imag = i_imag[0];
assign out1_real = i_real[1]; assign out1_imag = i_imag[1];
assign out2_real = i_real[2]; assign out2_imag = i_imag[2];
assign out3_real = i_real[3]; assign out3_imag = i_imag[3];
assign out4_real = i_real[4]; assign out4_imag = i_imag[4];
assign out5_real = i_real[5]; assign out5_imag = i_imag[5];
assign out6_real = i_real[6]; assign out6_imag = i_imag[6];
assign out7_real = i_real[7]; assign out7_imag = i_imag[7];

```



```
endmodule
```

FFT testbench:

```
`include "fft.v"
`timescale 1ns/1ps

module fft_tb();

    parameter CLOCK_PERIOD = 5; // 10 MHz clock

    reg sys_clk, sys_rst_n;
    reg write, start;

    reg signed [15:0] in0_real ,in0_imag;
    reg signed [15:0] in1_real ,in1_imag;
    reg signed [15:0] in2_real ,in2_imag;
    reg signed [15:0] in3_real ,in3_imag;
    reg signed [15:0] in4_real ,in4_imag;
    reg signed [15:0] in5_real ,in5_imag;
    reg signed [15:0] in6_real ,in6_imag;
    reg signed [15:0] in7_real ,in7_imag;
    wire ready;

    wire signed [15:0] out0_real ,out0_imag;
    wire signed [15:0] out1_real ,out1_imag;
    wire signed [15:0] out2_real ,out2_imag;
    wire signed [15:0] out3_real ,out3_imag;
    wire signed [15:0] out4_real ,out4_imag;
    wire signed [15:0] out5_real ,out5_imag;
    wire signed [15:0] out6_real ,out6_imag;
    wire signed [15:0] out7_real ,out7_imag;

    fft DUT(.CLK(sys_clk), .RST_N(sys_rst_n), .write(write), .start(start),
.in0_real(in0_real) ,.in0_imag(in0_imag), .in1_real(in1_real), .in1_imag(in1_imag),
.in2_real(in2_real) ,.in2_imag(in2_imag), .in3_real(in3_real) ,.in3_imag(in3_imag),
.in4_real(in4_real) ,.in4_imag(in4_imag), .in5_real(in5_real) ,.in5_imag(in5_imag),
.in6_real(in6_real) ,.in6_imag(in6_imag), .in7_real(in7_real) ,.in7_imag(in7_imag),
.ready(ready), .out0_real(out0_real) ,.out0_imag(out0_imag), .out1_real(out1_real),
.out1_imag(out1_imag), .out2_real(out2_real) ,.out2_imag(out2_imag), .out3_real(out3_real)
,.out3_imag(out3_imag), .out4_real(out4_real) ,.out4_imag(out4_imag),
.out5_real(out5_real) ,.out5_imag(out5_imag), .out6_real(out6_real) ,.out6_imag(out6_imag),
.out7_real(out7_real) ,.out7_imag(out7_imag));

    // VCD dump
    initial begin
        $dumpfile("fft.vcd");
        $dumpvars(0, DUT);
    end
end
```

```

// System clock generator
always begin
    #(CLOCK_PERIOD/2) sys_clk = ~sys_clk;
end

// Initial Condition
initial begin
    sys_clk = 1'b0; sys_rst_n = 1'b0;
    write = 1'b0; start = 1'b0;
    in0_real=16'h00_00 ;in0_imag = 0;
    in1_real=16'h01_00 ;in1_imag = 0;
    in2_real=16'h02_00 ;in2_imag = 0;
    in3_real=16'h03_00 ;in3_imag = 0;
    in4_real=16'h04_00 ;in4_imag = 0;
    in5_real=16'h05_00 ;in5_imag = 0;
    in6_real=16'h06_00 ;in6_imag = 0;
    in7_real=16'h07_00 ;in7_imag = 0;
    #CLOCK_PERIOD sys_rst_n = 1'b1;
    #CLOCK_PERIOD write = 1'b1;
    #CLOCK_PERIOD start = 1'b1;
    #CLOCK_PERIOD start = 1'b0;
    #(CLOCK_PERIOD/2) $display("START OF SIMULATION (Time: %g ns)", $time);
    #10000;
    $finish;
end

endmodule

```

synth.py

```

# read design
read_verilog fft.v
hierarchy -check
hierarchy -top fft
#flatten

# high level synthesis
proc; opt; clean
fsm; opt clean
memory; opt; clean

# low level synthesis
techmap; opt; clean

# map to target architecture
dfflibmap -liberty stdcells.lib
abc -liberty stdcells.lib

# split larger signals

```

splitnets -ports; opt; clean

write synthesis output

write_verilog synth.v

write_spice synth.sp

#print synthesis reports

stat

stat -liberty stdcells.lib

show -format svg -prefix /home/ujjwal/Desktop/ESDCS/ESDCS_project/syme fft

readme file:

ESDCS_FFT_Project

Project for the partial grading of Course: Efficient and Secure Digital Systems

Project Objectives


1. Design a digital circuit for Fast Fourier Transform (FFT) in Verilog
2. Create an appropriate test bench in Verilog to test the design
3. Simulate the design using Icarus Verilog and visualize the simulated VCD waveforms using GTKWave to verify functionality
4. Synthesize the design using Yosys with the Nangate Open Cell 45nm standard cell library in the typical TT corner
5. Analyze timing and power of the implementation using OpenSTA

Project Statement

- Input $x = \{x_0, x_1, \dots, x_7\}$
- Output $X = \{X_0, X_1, \dots, X_7\}$
- Output X is the 8-point FFT of input x
- Each input element x_m (for $m = 0, 1, \dots, 7$) is a complex number with real and imaginary parts each represented as a signed 16-bit fixed point quantity with 1 sign bit, 7 bits for decimal part and 8 bits for fractional part
- Each output element X_k (for $k = 0, 1, \dots, 7$) is a complex number with real and imaginary parts each represented as a signed 16-bit fixed-point quantity with 1 sign bit, 7 bits for decimal part and 8 bits for fractional part
- Additional Signals

CLK	Input	Clock	signal
RST_N	Input	Active-low	reset signal
write	Input	Input	write signal
start	Input	FFT computation	start signal
ready	Output	FFT computation	done signal

Synthesized Circuit:

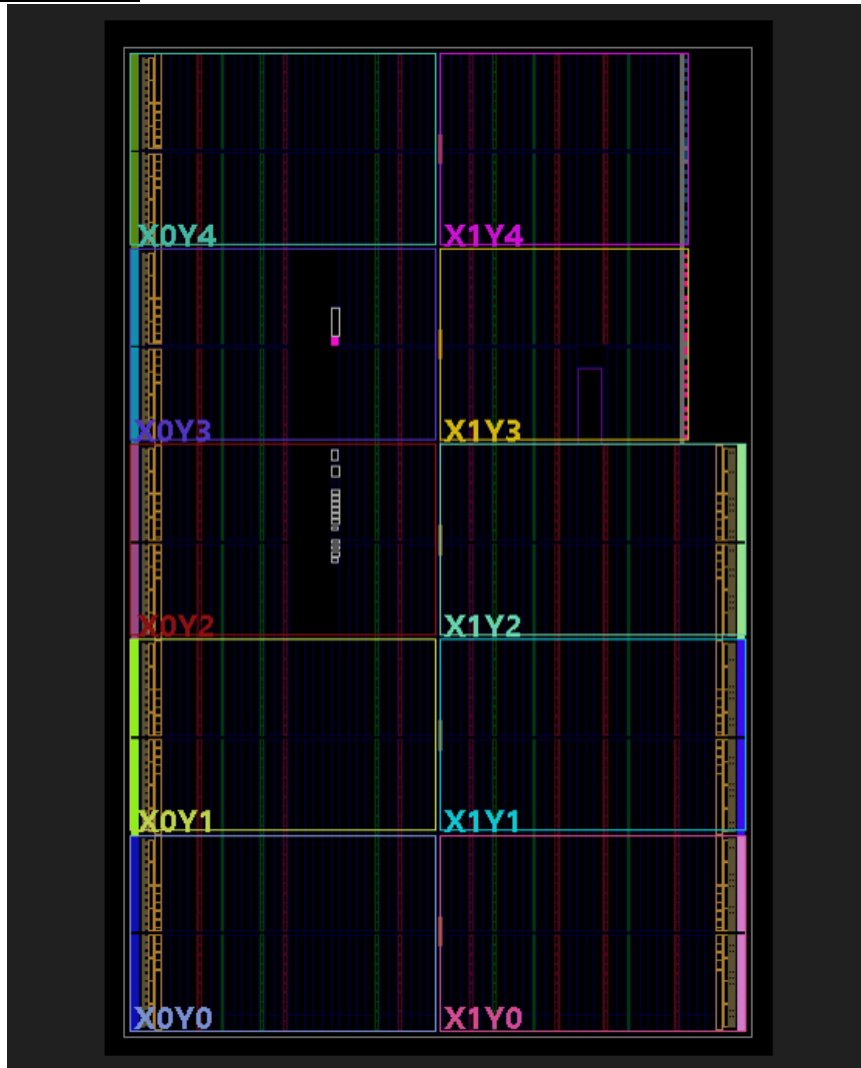

References

- [1] Wikipedia – Fast Fourier Transform
- [2] NPTEL – Hardware Modelling using Verilog by Prof. Indranil Sen Gupta
- [3] “The Fast Fourier Transform (FFT): Most Ingenious Algorithm Ever?” Youtube.com by Reducible
- [4] “DSP Tricks: Computing inverse FFTs using the forward FFT” – embedded.com